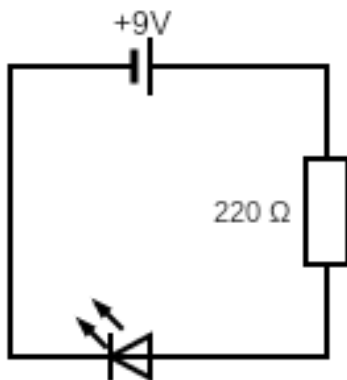


Basic Electronics Exercises: Resistor Circuits and Measurements

1. Basic Series Circuit

Setup:

- Build a circuit with a **9V source**, a **220Ω resistor**, and an **LED** (with series resistor for protection) like in the image below.



Tasks:

a) Calculate the theoretical current using Ohm's Law.

--

b) Measure resistance and voltage across the components using a multimeter.


c) Record values in a table:

Component	Measured Resistance (Ω)	Measured Voltage (V)	Theoretical Current (mA)
Resistor			
LED			
Whole Circuit			

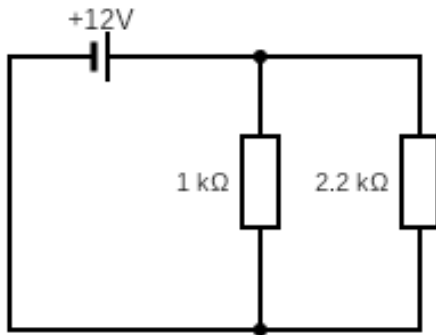2. Parallel Circuit

Setup:

- Build a circuit with a **12V source** and two parallel resistors: **1kΩ** and **2.2kΩ**.



Tasks:

- a) Calculate the equivalent resistance [$1 / R_{EQ} = 1 / R_1 + 1 / R_2$].

- b) Measure the equivalent resistance with the multimeter (**power off!**).

- c) Measure resistances and voltages, and compare with calculated values.

- d) Calculate total current and current through each resistor.

- e) Record values in a table:

Component	Measured Resistance (Ω)	Measured Voltage (V)	Theoretical Current (mA)	Measured Current (mA)
R1				
R2				
Whole Circuit				